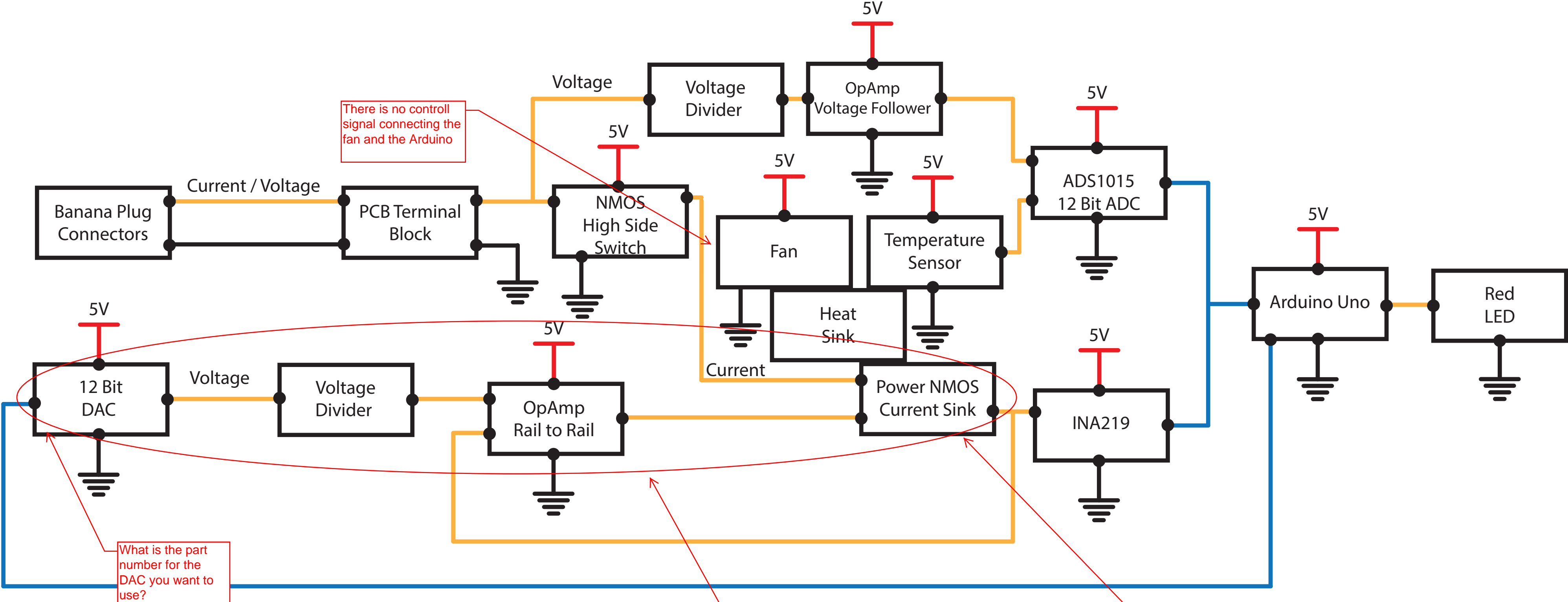


Arduino Electronic Load Hardware Block Diagram V02



Key

Digital

Ground

Analog

Power

This is great! I understand exactly what you are planning to do and the signal flow is clear.

You need a ground connection on the Current Sink

Arduino Electronic Load Hardware Block Diagram V02